

Chapter 5

Logic Design with MSI Components and Programmable Logic Devices

The complexity of a chip


Scale of integration:

- SSI 1 - 10 gates
- MSI 10 - 100 gates
- LSI 100 - 1000 gates
- VLSI > 1000 gates

Specialized MSI components

- adders
- comparators
- encoders/decoders
- multiplexers/demultiplexers


Half Adder

 


$$\text{sum} = x'y + xy'$$

$$\text{carry} = xy$$

Full Adder

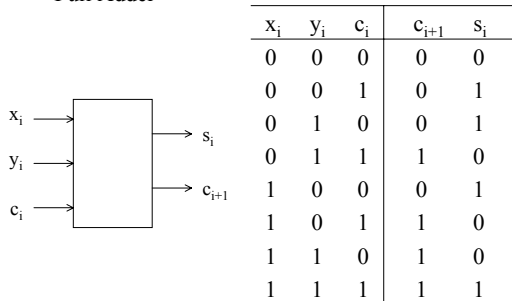

The Karnaugh maps for a full adder

 


SUM and CARRY functions

$$\text{SUM} = x'y'c + x'yc' + xy'c' + xyc$$

$$\text{CARRY} = xy + yc + cx$$

A realization of the binary full adder

 


Parallel (ripple) binary adder


Designed to add two binary numbers bit by bit



 Parallel binary subtracter constructed by using a parallel binary adder



Parallel binary adder/subtracter

 

Carry-look-ahead adder

- Problem: the time required to do addition is proportional to the number of bits involved.
- Solution: compute the carry for each stage independently by using a carry-look-ahead network.

Carry-Look-ahead Adder

Recall that

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i = x_i y_i + (x_i + y_i) c_i$$

Let $g_i = x_i y_i$ be the *carry-generate* function, and

$$p_i = x_i + y_i \text{ be the } \textit{carry-propagate} \text{ function.}$$

Then we can write $c_{i+1} = g_i + p_i c_i$ and

$$c_1 = g_0 + p_0 c_0$$


$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$


...

We see that all carry signal c_i can be computed by a two level logic circuit.

 
A carry lookahead adder. (a) General organization. (b) Sigma block




A 4-bit carry lookahead adder

 

 
Cascade connection of 4-bit carry lookahead adders




A 4-bit carry look-ahead generator

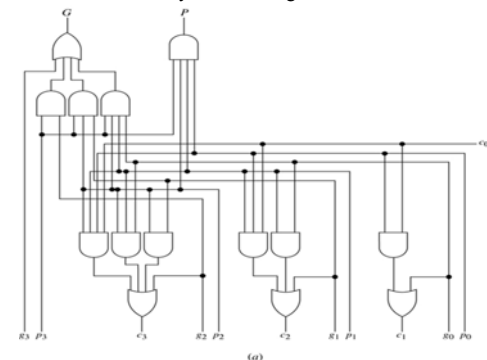

A 16-bit high-speed adder

 

 Organization of a single-decade decimal adder




J. C. Huang, 2004

Digital Logic Design

18

 Organization of a single-decade BCD adder




J. C. Huang, 2004

Digital Logic Design

19

A single-decade BCD adder

 


J. C. Huang, 2004

Digital Logic Design

20

Organization of a 1-bit comparator

 

J. C. Huang, 2004

Digital Logic Design

21

From the truth table (Table 5.4) on page 247 we obtained

$$G_{i+1} = A_i B_i' + A_i G_i + B_i' G_i$$

$$E_{i+1} = A_i' B_i' E_i + A_i B_i E_i$$


$$L_{i+1} = A_i' B_i + B_i L_i + A_i' L_i$$

J. C. Huang, 2004

Digital Logic Design

22






 
Comparing two binary numbers A and B . (a) 1-bit comparator network. (b) Cascade connection of 1-bit comparators.




J. C. Huang, 2004

Digital Logic Design


23

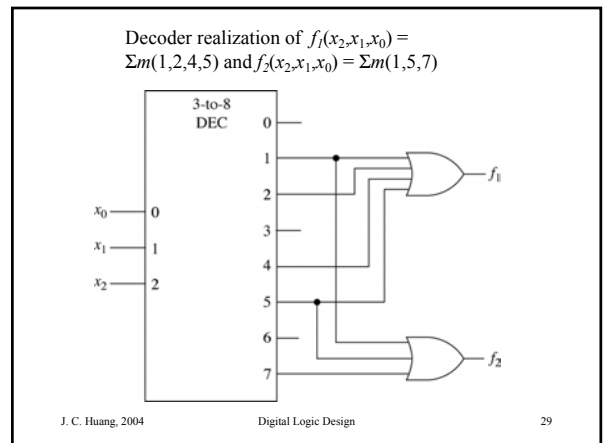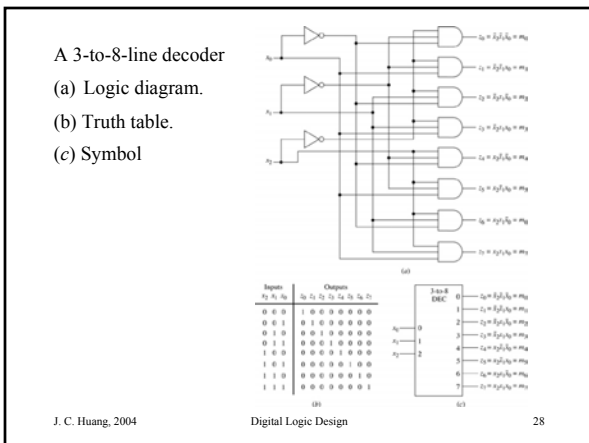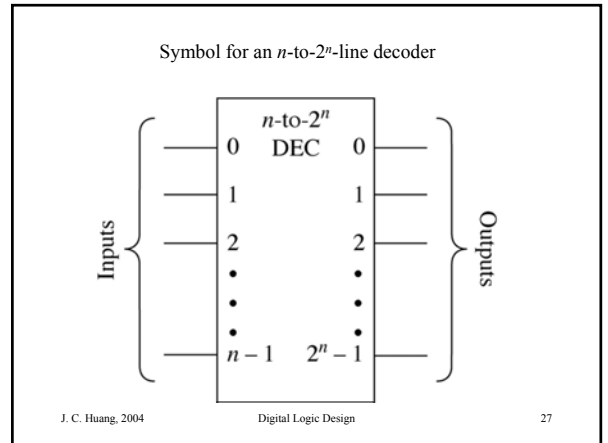 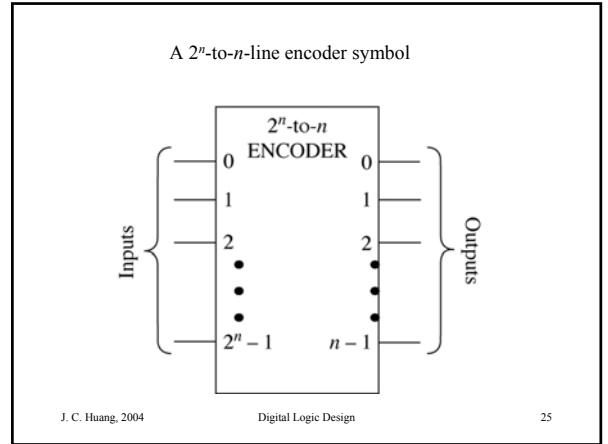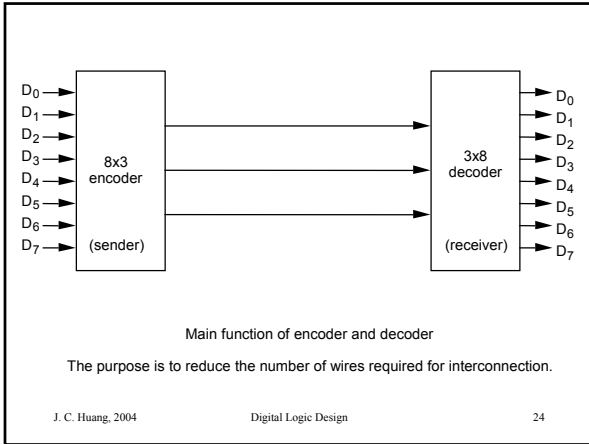

 
Decoder realization of Boolean functions
 $f_1 = \Pi M(2, 7)$ and $f_2 = \Pi M(0, 5, 7)$



 
A decoder realization of $f_1(x_2, x_1, x_0) = \Pi M(0, 1, 3, 5)$ and $f_2(x_2, x_1, x_0) = \Pi M(1, 3, 6, 7)$ (a) Using output or-gates. (b) Using output nor-gates.




A 3-to-8-line decoder using nand-gates

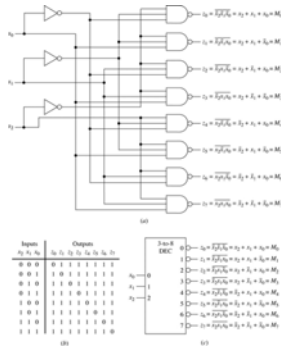

 
Realization of the pair of maxterm canonical expressions
 $f_1(x_2, x_1, x_0) = \Pi M(0, 3, 5)$ and $f_2(x_2, x_1, x_0) = \Pi M(2, 3, 4)$ with a 3-to-8-line decoder and two and-gates.



 
Realization of the Boolean expressions $f_1(x_2, x_1, x_0) = \Pi M(0, 1, 3, 4, 7)$ with a 3-to-8-line decoder and two nand-gates.



 A decoder realization of $f_1(x_2, x_1, x_0) = \Sigma m(0, 2, 6, 7)$ and $f_2(x_2, x_1, x_0) = \Sigma m(3, 5, 6, 7)$ (a) Using output and-gates. (b) Using output nand-gates.



 And-gate 2-to-4-line decoder with an enable input. (a) Logic diagram. (b) Compressed truth table. (c) Symbol.




J. C. Huang, 2004

Digital Logic Design

36

 Nand-gate 2-to-4-line decoder with an enable input




J. C. Huang, 2004

Digital Logic Design

37

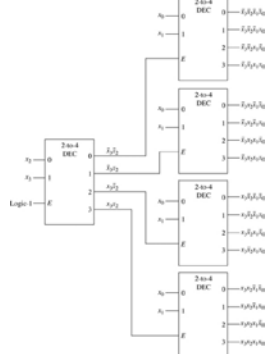
A 4-to-16-line decoder constructed from 2-to-4-line decoder



J. C. Huang, 2004

Digital Logic Design

38

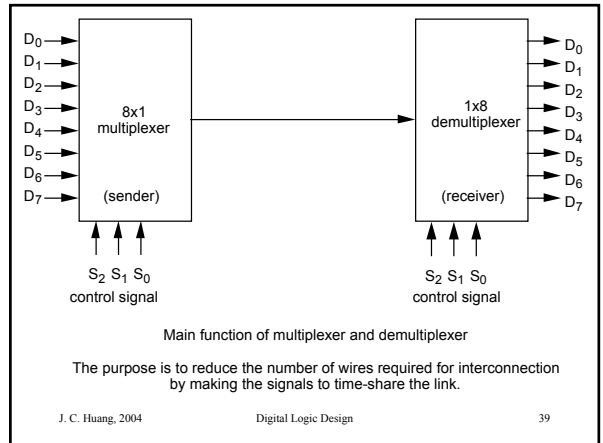


J. C. Huang, 2004

Digital Logic Design

39

 A multiplexer/demultiplexer arrangement for information transmission.




J. C. Huang, 2004

Digital Logic Design

40

A 4-to-1-line multiplexer

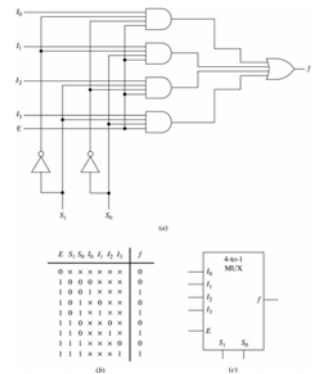


J. C. Huang, 2004


Digital Logic Design

41

Demultiplexer

 

A 2^n -to-1-line multiplexer symbol

 

MUX implementation of a Boolean function

- Any Boolean function of n variables can be implemented by a multiplexer with n control inputs in a straightforward manner.


Example: $f(x, y, z) = \Sigma m(2, 5, 6, 7)$

x	y	z	$f(x, y, z)$	$=$
0	0	0	$f(0, 0, 0)$	0
0	0	1	$f(0, 0, 1)$	0
0	1	0	$f(0, 1, 0)$	1
0	1	1	$f(0, 1, 1)$	0
1	0	0	$f(1, 0, 0)$	0
1	0	1	$f(1, 0, 1)$	1
1	1	0	$f(1, 1, 0)$	1
1	1	1	$f(1, 1, 1)$	1

MUX implementation of a Boolean function

- Even better, any Boolean function of n variables can be implemented by a multiplexer with $n-1$ control inputs as illustrated in the following.

 Implementing a function of 3 variables with a 4x1 MUX: Method 1



Using a multiplexer to implement a Boolean function: Method 1

Note that the output of a 4x1 multiplexer is

$$F(x, y, z) = x'y'I_0 + x'y'I_1 + xy'I_2 + xyI_3$$

Now, given a Boolean function


$$f(x, y, z) = f(0, 0, 0)x'y'z' + f(0, 1, 0)x'y'z + f(1, 0, 0)xy'z' + f(1, 1, 0)xyz' + f(0, 0, 1)x'y'z + f(0, 1, 1)x'yz + f(1, 0, 1)xy'z + f(1, 1, 1)xyz$$

The value for input I_0 is to be determined as follows.

if $f(0, 0, 0) =$	and $f(0, 0, 1) =$	then $f(0, 0, 0)x'y'z' + f(0, 0, 1)x'y'z =$	and thus we should let $I_0 =$
0	0	$0 = x'y'0$	0
0	1	$x'y'z$	z
1	0	$x'y'z'$	z'
1	1	$x'y' = x'y'1$	1

The value for I_1, I_2 , and I_3 are to be determined in a similar manner.

 Implementing a function of 3 variables with a 4x1 MUX: Method 2



Using a multiplexer to implement a Boolean function: Method 2

Note that the output of a 4x1 multiplexer is

$$F(x, y, z) = I_0y'z' + I_1y'z + I_2yz' + I_3yz$$

Now, given a Boolean function


$$f(x, y, z) = f(0, 0, 0)x'y'z' + f(0, 0, 1)x'y'z + f(0, 1, 0)xy'z' + f(0, 1, 1)xy'z + f(1, 0, 0)xy'z' + f(1, 0, 1)xy'z + f(1, 1, 0)xyz' + f(1, 1, 1)xyz$$

The value for input I_0 is to be determined as follows.

if $f(0, 0, 0) =$	and $f(0, 0, 1) =$	then $f(0, 0, 0)y'z' + f(0, 0, 1)y'z =$	and thus we should let $I_0 =$
0	0	$0 = 0y'z'$	0
0	1	$xy'z'$	x
1	0	$x'y'z'$	x'
1	1	$y'z' = 1y'z'$	1


The value for I_1, I_2 , and I_3 are to be determined in a similar manner.

 A multiplexer tree to form a 16-to-1-line multiplexer




Realization of a three-variable function using a 8-to-1-line multiplexer.

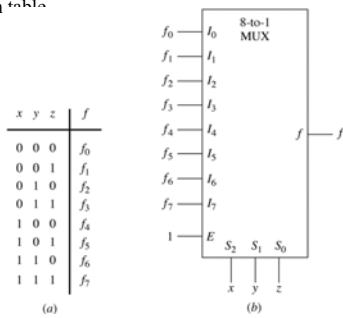
- (a) Three-variable truth table
(b) General realization.



 
Example: realization of $f(x,y,z) = \Sigma m(0,2,3,5)$



 Realizing a 3-variable Boolean function with a 4-to-1 multiplexer




 Realization of $f(x,y,z) = \Sigma m(0,2,3,5)$ using a 4-to-1-line multiplexer




Obtaining multiplexer realizations using Karnaugh maps.

 - (a) Cell groupings corresponding to the data line functions.
(b) Karnaugh maps for the I_i subfunctions.




Realization of $f(x,y,z) = \Sigma m(0,2,3,5)$.

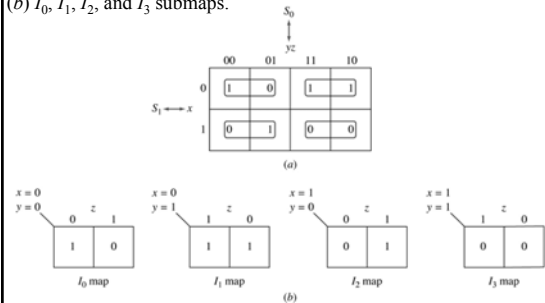- (a) Karnaugh map.
(b) I_0, I_1, I_2 , and I_3 submaps.




Using Karnaugh maps to obtain multiplexer realizations under various assignments to the select inputs.

 
- (a) Applying input variables y and z to the S_1 and S_0 select lines.
 (b) Applying input variables x and y to the S_0 and S_1 select lines.



 
Alternative realizations of $f(x,y,z) = \Sigma m(0,2,3,5)$.



 
A select line assignment and corresponding data line functions for a multiplexer realization of a four-variable function.



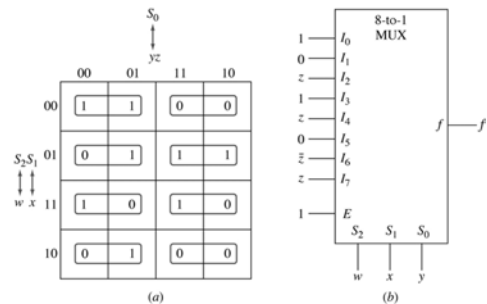
Realizations of $f(w,x,y,z) = \Sigma m(0,1,5,6,7,9,12,15)$.



 
Using a four-variable Karnaugh map to obtain a Boolean function realization with a 4-to-1-line multiplexer.



 
Realizations of the Boolean function $f(w,x,y,z) = \Sigma m(0,1,5,6,7,9,13,14)$.



 General structure of Programmable Logic Devices (PLDs)



 Buffer/inverter. (a) Symbol. (b) Logic equivalent




Types of PLDs


Device	AND-array	OR-array
PROM	Fixed	Programmable
PLA	Programmable	Programmable
PAL	Programmable	Fixed

Programming by blowing fuses.

 
(a) Before programming.
(b) After programming.




PLD notation

 

Structure of a PROM

 

 A $2^n \times m$ PROM.
 (a) Logic diagram.
 (b) Representation in PLD notation.




J. C. Huang, 2004

Digital Logic Design

72

 Using a PROM for logic design. (a) Truth table. (b) PROM realization.




J. C. Huang, 2004

Digital Logic Design

73

 Logic diagram of
 an $n \times p \times m$ PLA




J. C. Huang, 2004

Digital Logic Design

74

 Example of combinational logic design using a PLA. (a) Maps showing the multiple-output prime implicants. (b) Partial covering of the f_1 and f_2 maps. (c) Maps for the multiple-output minimal sum. (d) Realization using a $3 \times 4 \times 2$ PLA.




J. C. Huang, 2004

Digital Logic Design

75

 Example of combinational logic design using a PLA. (a) Maps showing the multiple-output prime implicants. (b) A multiple-output minimal sum covering. (c) Alternative multiple-output minimal sum covering. (d) Realization using a $3 \times 4 \times 2$ PLA.




J. C. Huang, 2004

Digital Logic Design

76

 Exclusive-or-gate with a programmable fuse.
 (a) Circuit diagram. (b) Symbolic representation.




J. C. Huang, 2004

Digital Logic Design

77

 General structure of a PLA having true and complemented output capability




J. C. Huang, 2004

Digital Logic Design

78

 Karnaugh maps for the functions $f_1(x,y,z) = \Sigma m(1,2,3,7)$ and $f_2(x,y,z) = \Sigma m(0,1,2,6)$




J. C. Huang, 2004

Digital Logic Design

79

 Two realizations of $f_1(x,y,z) = \Sigma m(1,2,3,7)$ and $f_2(x,y,z) = \Sigma m(0,1,2,6)$.




J. C. Huang, 2004

Digital Logic Design

80

 A simple four-input, three-output PAL device.




J. C. Huang, 2004

Digital Logic Design

81

 An example of using a PAL device to realize two Boolean functions. (a) Karnaugh maps. (b) Realization.



J. C. Huang, 2004

Digital Logic Design

82




A PLD programming unit

J. C. Huang, 2004

Digital Logic Design

83

 

A PLCC package with socket


Limitations of PLAs and PALs

These chips are limited to fairly modest size, typically supporting a combined number of inputs plus outputs of not more than 32.

Complex Programmable Logic Devices (CPLDs)


A CPLD comprises multiple PAL-like blocks on a single chip with internal wiring resources to connect the circuit blocks.

 It is made to implement complex circuits that cannot be done on a PAL or PLA.




Structure of a CPLD

A section of a CPLD

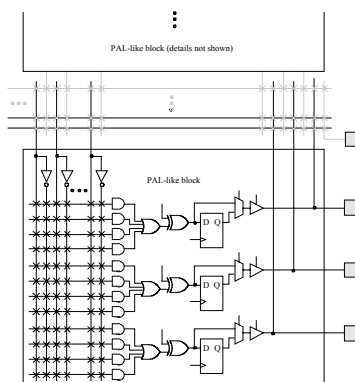

CPLD packaging and programming

 

A Measure of Circuit Size


A commonly used measure is the total number of two-input NAND gates that would be needed to build the circuit.

It is called the *number of equivalent gates*.

Field-Programmable Gate Arrays (FPGAs)

An FPGA is a PLD that supports implementation of large logic circuits.

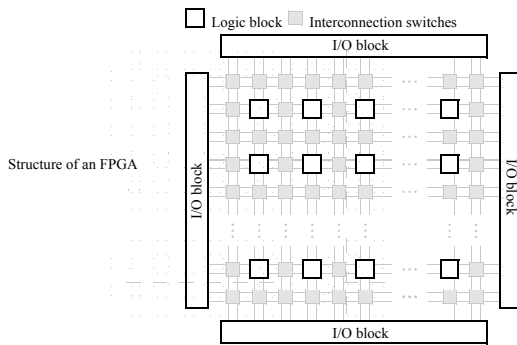It is different from others in that it does not contain AND or OR planes. Instead, it contains logic blocks as depicted in the next slide.




Typical FPGAs

FPGAs can be used to implement logic circuits of more than a few hundred thousand equivalent gates in size.


The most commonly used logic block is a *lookup table (LUT)* as depicted in Fig. 3.36.

Slide 3.35.1

A two-input lookup table

 

A three-input LUT

 

A section
of a
programmed
FPGA

