

## Chapter 6

### Flip-Flops and Simple Flip-Flop Applications

## Basic bistable element

- It is a circuit having two stable conditions (states).
- It can be used to store binary symbols.


## Flip-flops

A flip-flop is a bistable device, with inputs, that remains in a given state as long as power is applied and until input signals are applied to cause its output to change.

## Latches vs. flip-flops

- Latches are flip-flops for which the timing of the output changes are not controlled.
- For a latch, the output essentially responds immediately to changes on the input lines (and possibly the presence of a clock pulse).
- A flip-flop is designed to change its output at the edge of a controlling clock signal.


## SR (Set-Reset) latch

 


## Next state

- If Q denotes the present state of a memory device, i.e., the state at the time the input signals are applied, we shall use Q<sup>+</sup> or Q(t+1) to denote the *next state*, i.e., the new state assumed by the device in response to the input signals.


### R'S' latch

 

### Gated SR latch

 

### Gated D latch

 

## Timing considerations

- Propagation delays
- Minimum pulse width
- Setup and hold time

## Propagation delay

The time it takes a change in the input signal to produce a change in the output signal.

## Minimum pulse width


The minimum amount of time a signal must be applied in order to produce a desired result.

## Setup and hold times

- To achieve a satisfactory operation of a gated latch, constraints are normally placed on the time intervals between input changes.
- The minimum time the input signal must be held fixed before and after the latching action is called the *setup* time and *hold* time, respectively.
 
## JK- and T-type flip-flops

In addition to the SR-type and D-type flip-flops discussed above, there are two other types, viz., JK- and T-type flip-flops.




(a) Circuit

### JK flip-flop

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

(b) Truth table

 


(c) Graphical symbol

## JK flip-flops

A JK flip-flop works just like an SR flip-flop if we consider J input as S(et) input and K input as R(eset) input, except when both S and R inputs are set to 1, the output simply flips over.
 
## T-type flip-flops

A T flip-flop is obtained from a JK flip-flop by tying the J and K inputs together to form the T input.



## Flip-flops

- There are four different types of flip-flops: SR, D, JK, and T types.
- The properties of these flip-flops are summarized in the following 4 slides.
- The *function* and *application tables* are also known as *characteristic* and *excitation tables*, respectively.

SR-type flip-flop

Graphic symbol

$$Q(t+1) = S + R'Q$$

$$SR = 0$$

Characteristic equation

S	R	Q(t+1)
0	0	Q
0	1	0
1	0	1
1	1	?

Function table

Q	Q(t+1)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Application table

J. C. Huang, 2004
Digital Logic Design
18

D-type flip-flop

Graphic symbol

$$Q(t+1) = D$$

Characteristic equation

D	Q(t+1)
0	0
1	1

Function table

Q	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Application table

J. C. Huang, 2004
Digital Logic Design
19

JK-type flip-flop

Graphic symbol

$$Q(t+1) = JQ' + K'Q$$

Characteristic equation

J	K	Q(t+1)
0	0	Q
0	1	0
1	0	1
1	1	Q'

Function table

Q	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Application table

J. C. Huang, 2004
Digital Logic Design
20

T-type flip-flop

Graphic symbol

$$Q(t+1) = TQ' + T'Q$$

Characteristic equation

T	Q(t+1)
0	Q
1	Q'

Function table

Q	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

Application table

J. C. Huang, 2004
Digital Logic Design
21

## Positive and negative edge







- The transition of a control signal (clock pulse) from its low to high value (0 to 1) in positive logic is called the *positive edge* of the control signal, while the transition from high to low (1 to 0) is called the *negative edge*.

J. C. Huang, 2004
Digital Logic Design
22

      
## Edge-triggered flip-flops

- Edge triggered flip-flops use just one of the edges of the clock pulse to affect the reading of the input lines.
- These flip-flops are designed to be triggered by either the positive or negative edge.
- In analyzing the behavior of an asynchronous sequential circuit, one often needs to know which edge trigger the flip-flops used.


J. C. Huang, 2004
Digital Logic Design
23



### A 3-bit up-counter

 

(a) Circuit

 

(b) Timing diagram

The flip-flops are triggered by positive going edge of the clock input.


Analysis method:

Construct a list of state changes as follows.


1. Assume that the counter starts with some values, say, 000.
2. Because  $T=1$  for  $Q_0$ ,  $Q_0$  will change at the arrival of every clock pulse. Complete the listing for  $Q_0$ .
3. Because  $T=Q_0'$ , and because the flip-flop is triggered by a positive going clock input, for  $Q_1$ ,  $Q_1$  changes its content whenever  $Q_0$  changes from 1 to 0.
4. Do the same for the listing for  $Q_2$ .

$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0

### A 3-bit down-counter

 

(a) Circuit

 

(b) Timing diagram

The flip-flops are triggered by positive going edge of the clock input


Analysis method:

Construct a list of state changes as follows.

1. Assume that the counter starts with some values, say, 000.
2. Because  $T=1$  for  $Q_0$ ,  $Q_0$  will change at the arrival of every clock pulse. Complete the listing for  $Q_0$ .
3. Because  $T=Q_0$ , and because the flip-flop is triggered by a positive going clock input, for  $Q_1$ , it changes its content whenever  $Q_0$  changes from 0 to 1.
4. Do the same for the listing for  $Q_2$ .


$Q_2$	$Q_1$	$Q_0$
0	0	0
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

 The following synchronous counter can be analyzed similarly




$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
1	1	1
0	0	0

### Four-bit synchronous binary counter

 
 
### Four-bit synchronous binary counter variation




J. C. Huang, 2004

Digital Logic Design

36
 
### Four-bit synchronous binary counter with parallel load inputs




J. C. Huang, 2004

Digital Logic Design

37

### Synchronous mod-10 counter

 


$Q_3$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0
etc.			

J. C. Huang, 2004

Digital Logic Design

38
 
### 8-bit synchronous binary counter constructed from two 4-bit synchronous binary counters




J. C. Huang, 2004

Digital Logic Design

39

### Mod-4 ring counter

 


$Q_3$	$Q_2$	$Q_1$	$Q_0$
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
1	0	0	0
etc.			

J. C. Huang, 2004

Digital Logic Design

40
 
### Mod-8 twisted-ring counter (or Johnson counter)




$Q_3$	$Q_2$	$Q_1$	$Q_0$	And-gate inputs
0	0	0	0	$\overline{Q_3} \overline{Q_2} \overline{Q_1} \overline{Q_0}$
1	0	0	0	$Q_3 \overline{Q_2} \overline{Q_1} \overline{Q_0}$
1	1	0	0	$Q_3 Q_2 \overline{Q_1} \overline{Q_0}$
1	1	1	0	$Q_3 Q_2 Q_1 \overline{Q_0}$
1	1	1	1	$Q_3 Q_2 Q_1 Q_0$
0	1	1	1	$\overline{Q_3} Q_2 Q_1 Q_0$
0	0	1	1	$\overline{Q_3} \overline{Q_2} Q_1 Q_0$
0	0	0	1	$\overline{Q_3} \overline{Q_2} \overline{Q_1} Q_0$
0	0	0	0	$\overline{Q_3} \overline{Q_2} \overline{Q_1} \overline{Q_0}$
etc.				

J. C. Huang, 2004

Digital Logic Design

41


### Mod-7 twisted-ring counter

 

## Control signal generators

- A control signal generator is a sequential circuit that generate a sequence of bit patterns, each of which contains only one 1. It is used to activate various devices in turn.
- Shown in the next slide are the wave forms of 4-bit control signals.


### 4-bit control pulses

 


### Control-signal generator (continued)

There are three ways to generate control signals (with n bits):

 1. Use an n-bit ring counter (need n flip-flops)
2. Use a binary counter and a decoder ( need k flip-flops and n AND gates with k inputs, where  $n \leq 2^k$ )
3. Use a Johnson counter (need n/2 flip-flops) and n 2-input AND gates.



 A part of the control circuit for the processor



An n-bit Johnson counter, augmented with 2n AND-gates, will generate 2n-bit control signals. It uses n/2 flip-flops, 2n 2-input, AND gates.

Figure 7.30 Johnson counter


 


Figure 7.30 A 3-bit Johnson counter

Counting sequence of a 3-bit Johnson counter

A	B	C
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1
0	0	0

 

A Johnson counter, augmented with a bank of AND gates, becomes a control-signal generator

## Synchronous counters

A synchronous counter is a special kind of synchronous sequential circuit, the analysis and design of such a circuit will be discussed in the next chapter.