 



COSC3410

Analysis and Design of Sequential Circuits: Examples


J. C. Huang
Department of Computer Science
University of Houston



 The block diagram of a sequential circuit



 Block diagram for the sequential circuit shown in Fig. 6-16




$$\begin{aligned}
 JA &= B \\
 KA &= Bx' \\
 JB &= x' \\
 KB &= A'x + Ax'
 \end{aligned}$$

Sequential circuit implemented with JK flip-flops (Fig. 6-19)

An example analysis problem:

 Given the sequential circuit depicted below, construct the state table that describe its behavior.




$$\begin{aligned}
 JA &= B \\
 KA &= Bx' \\
 JB &= x' \\
 KB &= A'x + Ax'
 \end{aligned}$$

present state	next state	
	$x = 0$	$x = 1$
$A(t)B(t)$	$A(t+1)B(t+1)$	$A(t+1)B(t+1)$
0 0	?	?
0 1	?	?
1 0	?	?
1 1	?	?

Steps involved:

 1. Construct the truth table of the combinational network to determine the output and the input to the flip-flops.
2. Use the characteristic table of the flip-flops to determine the next states.



$$\begin{aligned}
 JA &= B \\
 KA &= Bx' \\
 JB &= x' \\
 KB &= A'x + Ax'
 \end{aligned}$$

Sequential circuit implemented with JK flip-flops (Fig. 6-19)

Step 1: construct the truth table of the combinational network.

x	A	B	JA	KA	JB	KB
0	0	0	0	0	1	0
0	0	1	1	1	1	0
0	1	0	0	0	1	1
0	1	1	1	1	1	1
1	0	0	0	0	0	1
1	0	1	1	0	0	1
1	1	0	0	0	0	0
1	1	1	1	0	0	0

Step 2: extend the truth table to includes contents of flip-flops at time $t+1$.

x	A	B	JA	KA	JB	KB	A(t+1)	B(t+1)
0	0	0	0	0	1	0		
0	0	1	1	1	1	0		
0	1	0	0	0	1	1		
0	1	1	1	1	1	1		
1	0	0	0	0	0	1		
1	0	1	1	0	0	1		
1	1	0	0	0	0	0		
1	1	1	1	0	0	0		

Step 2.1: find $A(t+1)$, with the help of a characteristic table.

x	A	B	JA	KA	JB	KB	$A(t+1)$	$B(t+1)$
0	0	0	0	0	1	0	0	
0	0	1	1	1	1	0	1	
0	1	0	0	0	1	1	1	
0	1	1	1	1	1	1	0	
1	0	0	0	0	0	1	0	
1	0	1	1	0	0	1	1	
1	1	0	0	0	0	0	1	
1	1	1	1	0	0	0	1	

The characteristic table of a JK flip-flop

J K	$Q(t+1)$	
0 0	$Q(t)$	no change
0 1	0	reset
1 0	1	set
1 1	$Q'(t)$	complement

Step 2.2: find $B(t+1)$, with the help of a characteristic table.

x	A	B	JA	KA	JB	KB	A(t+1)	B(t+1)
0	0	0	0	0	1	0	0	1
0	0	1	1	1	1	0	1	1
0	1	0	0	0	1	1	1	1
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	1	0	0	1	1	0
1	1	0	0	0	0	0	1	0
1	1	1	1	0	0	0	1	1

The characteristic table of a JK flip-flop

J K	Q(t+1)	
0 0	Q(t)	no change
0 1	0	reset
1 0	1	set
1 1	Q'(t)	complement

Step 2.3: final step.

x	A	B	JA	KA	JB	KB	A(t+1)	B(t+1)
0	0	0	0	0	1	0	0	1
0	0	1	1	1	1	0	1	1
0	1	0	0	0	1	1	1	1
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	1	0	0	1	1	0
1	1	0	0	0	0	0	1	0
1	1	1	1	0	0	0	1	1

Reconstruct the state table to yield

present state	next state	
	x = 0	x = 1
A(t)B(t) 0 0	A(t+1)B(t+1) 0 1	A(t+1)B(t+1) 0 0
0 1	1 1	1 0
1 0	1 1	1 0
1 1	0 0	1 1

Mealy and Moore Models

There are two models of sequential circuit:

Mealy Model: the outputs are functions of both the present states and inputs.

Moore Model: the outputs are a function of the present state only.

Example:

State Reduction

Two states are said to be equivalent if, for each possible single input, they give exactly the same output and send the circuit either to the same state or to an equivalent state.

When two states are equivalent in this sense, one of them can be removed without altering the input-output relations.

Design Steps

1. Obtain the word description of the desired circuit behavior.
2. Construct the state table of the desired circuit.
3. Reduce the number of state to the extent possible (state reduction).
4. Assign a bit pattern to each state (state assignment).
5. Determine the no. of flip-flops needed and assign a letter symbol to each.
6. Choose the type of flip-flop to be used.
7. Derive the truth table of the required combinational circuit from the state table.
8. Simplify the combinational circuit.
9. Draw the logic diagram.

Design Example:

Suppose we are given a word description of the desired circuit behavior, and it is translated into the following state table (Step 2):

present state	next state		output	
	x=0	x=1	x=0	x=1
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	g	d	0	1
g	g	h	0	1
h	g	a	1	0

Design Example:

The number of state can be reduced to 4 (Step 3):

present state	next state		output	
	x=0	x=1	x=0	x=1
a	f	b	0	0
b	d	a	0	0
d	f	a	1	0
f	f	a	0	0
		d		1
		d		

Design Example:

The reduced state table (State 3):

present state	next state		output	
	x=0	x=1	x=0	x=1
a	f	b	0	0
b	d	a	0	0
d	f	a	1	0
f	f	d	0	1

Design Example:

A possible state assignment (State 4):

present state	next state		output	
	x=0	x=1	x=0	x=1
a	f	b	0	0
b	d	a	0	0
d	f	a	1	0
f	f	d	0	1

00 → a

01 → b


10 → d

11 → f

present state	next state		output	
	x=0	x=1	x=0	x=1
A B	A(t+1)B(t+1)	A(t+1)B(t+1)	y(t)	y(t)
0 0	1 1	0 1	0	0
0 1	1 0	0 0	0	0
1 0	1 1	0 0	1	0
1 1	1 1	1 0	0	1

Design Example

 This state table can be implemented by a sequential circuit of the form depicted below using D type flip-flops (Steps 5 and 6):



Reconstruct the state table

present state	next state		output	
	x=0	x=1	x=0	x=1
A B	A(t+1)B(t+1)	A(t+1)B(t+1)	y(t)	y(t)
0 0	1 1	0 1	0	0
0 1	1 0	0 0	0	0
1 0	1 1	0 0	1	0
1 1	1 1	1 0	0	1

in preparation for expanding it into a truth table of the combinational network required (Step 7):

x	A(t)	B(t)	A(t+1)	B(t+1)	y(t)
0	0	0	1	1	0
0	0	1	1	0	0
0	1	0	1	1	1
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	1	0	1

Expand the state table into the truth table of the combinational network (Step 7):

x	A(t)	B(t)	A(t+1)	B(t+1)	DA	DB	y(t)
0	0	0	1	1	1		0
0	0	1	1	0	1		0
0	1	0	1	1	1		1
0	1	1	1	1	1		0
1	0	0	0	1	0		0
1	0	1	0	0	0		0
1	1	0	0	0	0		0
1	1	1	1	0	1		1

Excitation table of a D type flip-flop

Q(t)	Q(t+1)	D(t)
0	0	0
0	1	1
1	0	0
1	1	1

Expand the state table into the truth table of the combinational network (Step 7):

x	A(t)	B(t)	A(t+1)	B(t+1)	DA	DB	y(t)
0	0	0	1	1	1	1	0
0	0	1	1	0	1	0	0
0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	0
1	0	1	0	0	0	0	0
1	1	0	0	0	0	0	0
1	1	1	1	0	1	0	1

Excitation table of a D type flip-flop

Q(t)	Q(t+1)	D(t)
0	0	0
0	1	1
1	0	0
1	1	1

Simplify the Boolean functions that describe the outputs of the combinational network (Step 8):

	A'B'	A'B	AB	AB'
x'	1	1	1	1
x	0	0	1	0

$$DA = x' + AB$$

	A'B'	A'B	AB	AB'
x'	1	0	1	1
x	1	0	0	0


$$DB = x'A + A'B'$$

	A'B'	A'B	AB	AB'
x'	0	0	0	1
x	0	0	1	0

$$y = x'AB' + xAB$$

Design Example

 This state table can be implemented by a sequential circuit of the form depicted below using JK flip-flops (Steps 5 and 6):



Again, start with the state table:

x	A(t)	B(t)	A(t+1)	B(t+1)	y(t)
0	0	0	1	1	0
0	0	1	1	0	0
0	1	0	1	1	1
0	1	1	1	1	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	1	0	1

In preparation for constructing the truth table of the required combinational circuit, expand the state table to include the columns for inputs to the flip-flops:

x	A(t)	B(t)	A(t+1)	B(t+1)	JA	KA	JB	KB	y(t)
0	0	0	1	1					0
0	0	1	1	0					0
0	1	0	1	1					1
0	1	1	1	1					0
1	0	0	0	1					0
1	0	1	0	0					0
1	1	0	0	0					0
1	1	1	1	0					1

With the help of an excitation table find inputs to flip-flop A (Step 7):

x	A(t)	B(t)	A(t+1)	B(t+1)	JA	KA	JB	KB	y(t)
0	0	0	1	1	1	X			0
0	0	1	1	0	1	X			0
0	1	0	1	1	X	0			1
0	1	1	1	1	X	0			0
1	0	0	0	1	0	X			0
1	0	1	0	0	0	X			0
1	1	0	0	0	X	1			0
1	1	1	1	0	X	0			1

Excitation table of a JK flip-flop

Q(t)	Q(t+1)	J(t)	K(t)
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

With the help of an excitation table find inputs to flip-flop B (Step 7):

x	A(t)	B(t)	A(t+1)	B(t+1)	JA	KA	JB	KB	y(t)
0	0	0	1	1	1	X	1	X	0
0	0	1	1	0	1	X	X	1	0
0	1	0	1	1	X	0	1	X	1
0	1	1	1	1	X	0	X	0	0
1	0	0	0	1	0	X	1	X	0
1	0	1	0	0	0	X	X	1	0
1	1	0	0	0	X	1	0	X	0
1	1	1	1	0	X	0	X	1	1

Excitation table of a JK flip-flop

Q(t)	Q(t+1)	J(t)	K(t)
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Simplify the outputs of the combinational network (Step 8):

	A'B'	A'B	AB	AB'
x'	1	1	X	X
x	0	0	X	X

$$JA = x'$$

	A'B'	A'B	AB	AB'
x'	X	X	0	0
x	X	X	0	1

$$KA = xB'$$

	A'B'	A'B	AB	AB'
x'	1	X	X	1
x	1	X	X	0

$$JB = x' + A'$$

	A'B'	A'B	AB	AB'
x'	X	1	0	X
x	X	1	1	X

$$KB = x + A'$$

	A'B'	A'B	AB	AB'
x'	0	0	0	1
x	0	0	1	0


$$y = x'AB' + xAB$$

Design of a 4-bit synchronous up counter

The state table

present state (at time t)	next state (at t+1)
A ₄ A ₃ A ₂ A ₁	A ₄ A ₃ A ₂ A ₁
0 0 0 0	0 0 0 1
0 0 0 1	0 0 1 0
0 0 1 0	0 0 1 1
0 0 1 1	0 1 0 0
0 1 0 0	0 1 0 1
0 1 0 1	0 1 1 0
0 1 1 0	0 1 1 1
0 1 1 1	1 0 0 0
1 0 0 0	1 0 0 1
1 0 0 1	1 0 1 0
1 0 1 0	1 0 1 1
1 0 1 1	1 1 0 0
1 1 0 0	1 1 0 1
1 1 0 1	1 1 1 0
1 1 1 0	1 1 1 1
1 1 1 1	0 0 0 0

The block diagram

 

The excitation function for the four JK flip-flops

present state (at time t)	next state (at t+1)	JA ₁	KA ₁	JA ₂	KA ₂	JA ₃	KA ₃	JA ₄	KA ₄
A ₄ A ₃ A ₂ A ₁	A ₄ A ₃ A ₂ A ₁								
0 0 0 0	0 0 0 1	1	X	0	X	0	X	0	X
0 0 0 1	0 0 1 0	X	1	1	X	0	X	0	X
0 0 1 0	0 0 1 1	1	X	X	0	0	X	0	X
0 0 1 1	0 1 0 0	X	1	X	1	1	X	0	X
0 1 0 0	0 1 0 1	1	X	0	X	X	0	0	X
0 1 0 1	0 1 1 0	X	1	1	X	X	0	0	X
0 1 1 0	0 1 1 1	1	X	X	0	X	0	0	X
0 1 1 1	1 0 0 0	X	1	X	1	X	1	1	X
1 0 0 0	1 0 0 1	1	X	0	X	0	X	X	0
1 0 0 1	1 0 1 0	X	1	1	X	0	X	X	0
1 0 1 0	1 0 1 1	1	X	X	0	0	X	X	0
1 0 1 1	1 1 0 0	X	1	X	1	1	X	X	0
1 1 0 0	1 1 0 1	1	X	0	X	X	0	X	0
1 1 0 1	1 1 1 0	X	1	1	X	X	0	X	0
1 1 1 0	1 1 1 1	1	X	X	0	X	0	X	0
1 1 1 1	0 0 0 0	X	1	X	1	X	1	X	1

From the truth table we see that the desired inputs to the flip-flops can be simplified to

$$JA_1 = 1$$

$$KA_1 = 1$$

$$JA_2 = A_1$$

$$KA_2 = A_1$$

$$JA_3 = A_2A_1$$

$$KA_3 = A_2A_1$$

$$JA_4 = A_3A_2A_1$$

$$KA_4 = A_3A_2A_1$$

and hence the logic diagram shown in Fig. 7-17.

Note that if we let $JA_1 = KA_1 = 0$ then none of the flip-flop will change its state, and therefore we can use it to stop (i.e., to disable) the counter.

Design of a 4-bit synchronous **down** counter

The state table

present state (at time t)	next state (at t+1)
A ₄ A ₃ A ₂ A ₁	A ₄ A ₃ A ₂ A ₁
0 0 0 0	1 1 1 1
0 0 0 1	0 0 0 0
0 0 1 0	0 0 0 1
0 0 1 1	0 0 1 0
0 1 0 0	0 0 1 1
0 1 0 1	0 1 0 0
0 1 1 0	0 1 0 1
0 1 1 1	0 1 1 0
1 0 0 0	0 1 1 1
1 0 0 1	1 0 0 0
1 0 1 0	1 0 0 1
1 0 1 1	1 0 1 0
1 1 0 0	1 0 1 1
1 1 0 1	1 1 0 0
1 1 1 0	1 1 0 1
1 1 1 1	1 1 1 0

The excitation function for the four JK flip-flops

present state (at time t)	next state (at t+1)	JA ₁	KA ₁	JA ₂	KA ₂	JA ₃	KA ₃	JA ₄	KA ₄
A ₄ A ₃ A ₂ A ₁	A ₄ A ₃ A ₂ A ₁								
0 0 0 0	1 1 1 1	1	X	1	X	1	X	1	X
0 0 0 1	0 0 0 0	X	1	0	X	0	X	0	X
0 0 1 0	0 0 0 1	1	X	X	1	0	X	0	X
0 0 1 1	0 0 1 0	X	1	X	0	0	X	0	X
0 1 0 0	0 0 1 1	1	X	1	X	X	1	0	X
0 1 0 1	0 1 0 0	X	1	0	X	X	0	0	X
0 1 1 0	0 1 0 1	1	X	X	1	X	0	0	X
0 1 1 1	0 1 1 0	X	1	X	0	X	0	0	X
1 0 0 0	0 1 1 1	1	X	1	X	1	X	X	1
1 0 0 1	1 0 0 0	X	1	0	X	0	X	X	0
1 0 1 0	1 0 0 1	1	X	X	1	0	X	X	0
1 0 1 1	1 0 1 0	X	1	X	0	0	X	X	0
1 1 0 0	1 0 1 1	1	X	1	X	X	1	X	0
1 1 0 1	1 1 0 0	X	1	0	X	X	0	X	0
1 1 1 0	1 1 0 1	1	X	X	1	X	0	X	0
1 1 1 1	1 1 1 0	X	1	X	0	X	0	X	0

From the truth table we see that the desired inputs to the flip-flops can be simplified to

$$JA_1 = 1$$

$$KA_1 = 1$$

$$JA_2 = A'_1$$

$$KA_2 = A'_1$$

$$JA_3 = A'_2A'_1$$

$$KA_3 = A'_2A'_1$$

$$JA_4 = A'_3A'_2A'_1$$

$$KA_4 = A'_3A'_2A'_1$$

This is reflected in the logic diagram shown in Fig. 7-18. Note that this design can be directly translated into a T flip-flop implementation because the J input to every flip-flop is identical to its K input.